

- (b) For the circuit shown in figure 2, determine 10
- a) D.C output voltage
 - b) Rectification Efficiency
 - c) Peak Inverse Voltage
 - d) Output frequency
- Assume the diodes are ideal

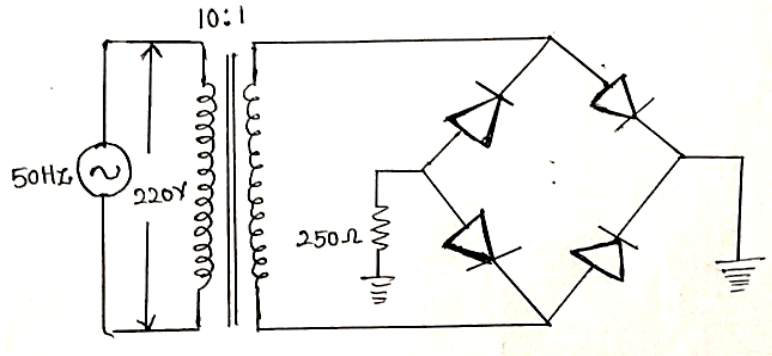


Fig.2

- 3 (a) The introduction of MOSFET device has brought a change in the domain of switching in Electronics. Identify the MOSFET which initially has no channel between drain and source in its construction. For the same, elaborate the working principle, drain characteristics and transfer characteristics with neat diagrams. 10

OR

- (b) Explain how a full adder can be built using two half adders. 10

PART - B (20 Marks)

- 4 A closed magnetic circuit of cast steel contains a 6cm long path of cross-sectional area 1 cm^2 and a 2 cm path of cross-sectional area 0.5 cm^2 . A coil of 200 turns is wound around the 6cm length of the circuit and a current of 0.4A flows through it. Determine the flux density in the 2cm path of the magnetic circuit. Relative permeability of cast steel is 750. 10
- 5 Design a 4-bit ripple counter and give an explanation of its operation with neat signal diagram. 10

