

Reg. No.:

Name :



**VIT**<sup>®</sup>  
**BHOPAL**  
www.vitbhopal.ac.in

**TERM END EXAMINATIONS (TEE) – December 2021- January 2022**

Programme	: B.Tech (CSE) [BHI,BCE,BEC,BCY]	Semester	: Fall 2021-22
Course Name	: Electric Circuits and Systems	Course Code	: EEE1001
Faculty Name	: Dr. Praveen Shukla	Slot / Class No	: F11+ F12+F13/0071
Time	: 1½ hours	Max. Marks	: 50

**Answer ALL the Questions**

Q.No. Question Description Marks

**PART - A ( 30 Marks)**

- 1 (a) For the circuit shown in the Fig.1 the thevenin equivalent voltage (in Volts) across terminals a-b is \_\_\_\_\_.

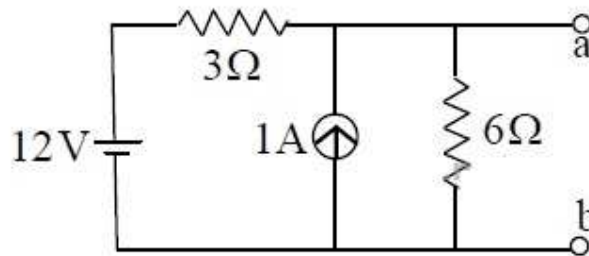


Fig.1

OR

- (b) In circuit fig .2 shown, switch SW is closed at  $t = 0$ . Assuming zero initial conditions, the value of  $V_c(t)$  (in volts) at  $t = 1$  second is \_\_\_\_\_

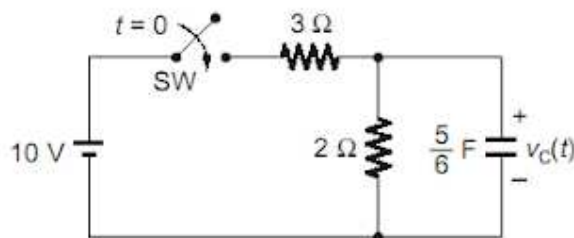


Fig.2

- 2 (a) Write a working principal of D.C. motor. Derive the voltage, power and torque equation for D.C. Motor. What are the different types of Speed control D.C. Motor?

OR

- (b) What is a zener diode? How is it different from a p-n junction diode?

- 3 (a) In BJT, the reverse saturation current of the collector base junction is 15 nA at low collector voltages. 10
- I. If the current amplification factor is 0.98, then the collector current with emitter open is \_\_\_\_\_
  - II. In the above problem if the current amplification factor increases by 1%, then the changes in the collector current with base open is \_\_\_\_\_

OR

- (b) In the 4×1 multiplexer Fig.3, the output of the multiplexer F is \_\_\_\_\_ 10

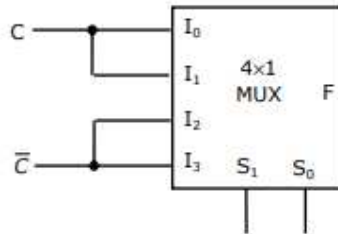


Fig. 3

**PART - B (20 Marks)**

- 4 Two inductors whose self-inductances are of 75mH and 55mH respectively are connected together in parallel aiding. Their mutual inductance is given as 22.5mH. Calculate the total inductance of the parallel combination. 10
- 5 Draw S-R FF using NAND gate, explain its operation 10

